

MAHARAJA RANJIT SINGH PUNJAB TECHNICAL UNIVERSITY, BATHINDA
ANSWER KEY ELECTRICAL ENGINEERING

1. c
2. d
3. d
4. a
5. c
6. d
7. d
8. d
9. d
10. b
11. b
12. b
13. c
14. b
15. a
16. c
17. d
18. d
19. b
20. c
21. a
22. b
23. b
24. c
25. c
26. b
27. b
28. d
29. a
30. d
31. b
32. b
33. b
34. a
35. a
36. b
37. b
38. c
39. d
40. b

Rabind
14/1/25
Controller of Examinations
MRSPTU, Bathinda

MAHARAJA RANJIT SINGH PUNJAB TECHNICAL UNIVERSITY, BATHINDA
Ph.D. Entrance Examination of ELECTRICAL ENGINEERING

Q1. The Eigen values of the matrix $\begin{bmatrix} 4 & -2 \\ -2 & 1 \end{bmatrix}$

- a) are 1 and -4
- b) are -1 and 2
- c) are 0 and 5
- d) cannot be determined

Q2. The optimum value of function $f(x) = x^2 - 4x + 2$ is

- a) 2(maximum)
- b) 2(minimum)
- c) -2(maximum)
- d) -2(minimum)

Q3. A class of first year B.Tech students is composed of four batches A,B,C and D, each consisting of 30 students. It is found that the sessional marks of students in Basic Electrical Engineering in batch C have a mean of 6.6 and standard deviation of 2.3. The mean and standard deviation of marks for the entire class are 5.5 and 4.2 respectively. It is decided by course instructor to normalize the marks of the students of all batches to have the same mean and standard deviation as that of entire class. Due to this, the marks of the student in batch C are changed from 8.5 to

- a) 6.0
- b) 7.0
- c) 8.0
- d) 9.0

Q4. If $f(t) = F(s)$, then $f(t-T)$ is

- a) $e^{sT}F(S)$
- b) $e^{-sT}F(S)$
- c) $F(s)/1+e^{sT}$
- d) $F(s)/1-e^{-sT}$

Q5. Superposition Theorem is not applicable to

- a) Voltage Calculations
- b) Bilateral Elements
- c) Power Calculations
- d) Passive elements

Q6. How many 200W/220V incandescent lamps connected in series would consume same total power as a single 100W/220V incandescent lamp?

- a) not possible
- b) 4
- c) 3
- d) 2

Q7. Which of the following are conditions for a two port network to be reciprocal one?

1. $Z_{12} = Z_{21}$ 2. $Y_{12} = Y_{21}$ 3. $h_{12} = -h_{21}$

Select the correct conditions from the code given below:

- a) Only 1 and 2
- b) Only 2 and 3
- c) Only 1 and 3
- d) 1, 2 and 3

- Q24. If $u(t)$, $r(t)$ denote the unit step and unit ramp functions respectively and $u(t)*r(t)$ their convolution, then the function $u(t+1)*r(t-2)$ is given by:
- $(1/2)(t-1)(t-2)$
 - $(1/2)(t-1)u(t-2)$
 - $(1/2)(t-1)^2 u(t-1)$
 - None of the above
- Q25. At an industrial sub-station with a 4MW load, a capacitor of 2MVAR is installed to maintain the load factor at 0.97 lagging. If the capacitor goes out of service, the load power factor becomes
- 0.85 lag
 - 1.00
 - 0.80lag
 - 0.90lag
- Q26. Choose the appropriate auxiliary components of HVDC transmission system from following
- DC line inductor
 - AC line inductor
 - Reactive Power sources
 - distance relays on DC line
 - Series capacitance on AC lines
- Only 1 and 2
 - Only 1 and 3
 - Only 2 and 4
 - Only 4 and 5
- Q27. The neutral of 10MVA, 11kV alternator is earthed through a resistance of 5ohms. The earth fault relay is set to operate at 0.75A. The CT's have a ratio of 1000/5. what percentage of alternator winding is protected?
- 85%
 - 88.2%
 - 15%
 - 11.8%
- Q28. The parameters of transposed overhead transmission line are given as: self reactance $X_s=0.4\Omega/\text{km}$ and mutual reactance $X_m= 0.1\Omega/\text{km}$. The positive sequence reactance X_1 and zero sequence reactance X_0 respectively in Ω/km are
- 0.3, 0.2
 - 0.5, 0.2
 - 0.5, 0.6
 - 0.3, 0.6
- Q29. The effect of stray magnetic fields on the actuating torque of a portable instrument is maximum when the operating field of the instrument and stray fields are
- perpendicular
 - parallel
 - inclined at 60°
 - inclined at 30°
- Q30. An average reading digital multimeter reads 10V when fed with a triangular wave, symmetric about the time axis. For the same input an rms reading meter will read:
- $20/\sqrt{3}$
 - $10/\sqrt{3}$
 - $20\sqrt{3}$
 - $10\sqrt{3}$

- Q31. A 500/5A, 50Hz current transformer has a bar primary. The secondary burden is a pure resistance of 1Ω and it draws a current of 5A. If the magnetic core requires 250AT for magnetization, the percentage error is
- 10.56
 - 10.56
 - 11.80
 - 11.80
- Q32. The simultaneous application of signals $x(t)$ and $y(t)$ to the horizontal and vertical plates respectively of an oscilloscope, produces a vertical figure of 8 display. If P and Q are constants and $x(t) = P\sin(4t+30)$, then $y(t)$ is equal to
- $Q\sin(4t-30)$
 - $Q\sin(2t+15)$
 - $Q\sin(8t+60)$
 - $Q\sin(4t+30)$
- Q33. A three phase diode bridge rectifier is fed from a 400V RMS 50Hz three phase AC source. If the load is purely resistive, then peak instantaneous output voltage is equal to
- 400V
 - $400\sqrt{2}$ V
 - $400\sqrt{2/3}$
 - $400\sqrt{3}$
- Q34. A step down chopper is operated in the continuous conduction mode in steady state with a constant duty ratio D. If V_0 is the magnitude of dc output voltage and if V_s is the magnitude of dc input voltage, the ratio of V_0/V_s is given as:
- D
 - 1-D
 - $1/(1-D)$
 - $D/(1-D)$
- Q35. A three phase 440V 50Hz AC mains fed thyristor bridge is feeding a 440V Dc, 15kW 1500rpm separately excited dc motor with a ripple free continuous current in dc link under all operating conditions, neglecting losses, the power factor of the ac mains at half the rated speed is
- 0.354
 - 0.372
 - 0.90
 - 0.955
- Q36. A 3 phase voltage source inverter is operated in 180° conduction mode. Which one of the following statements is true?
- Both pole- voltage and line voltage will have 3rd harmonic components
 - Pole voltage will have 3rd harmonic component but line voltage will be free from 3rd harmonic
 - Line voltage will have 3rd harmonic component but pole voltage will be free from 3rd harmonic
 - Both pole- voltage and line voltage will be free from 3rd harmonic components
- Q37. The output Y of a 2 bit comparator is logic 1 whenever 2 bit input A is greater than 2 bit input B. The number of combinations for which the output is logic 1 is
- 4
 - 6
 - 8
 - 10

- Q38. A bulb in a stair case has two switches one switch being at ground floor and other one at first floor. The bulb can be turned ON and also can be turned OFF by any one of the switches irrespective of the state of the other switch. The logic of switching of bulb resembles
- a) AND gate
 - b) OR gate
 - c) XOR gate
 - d) NAND gate
- Q39. A low pass filter with a cut off frequency as 30Hz is cascaded with a high pass filter with a cut off frequency of 20Hz. The resultant system of filters function as
- a) all pass filter
 - b) all stop filter
 - c) band stop filter
 - d) band pass filter
- Q40. In a common emitter amplifier the un bypassed emitter resistance provides
- a) Voltage shunt feedback
 - b) Current series feedback
 - c) Negative voltage feedback
 - d) Positive current feedback